
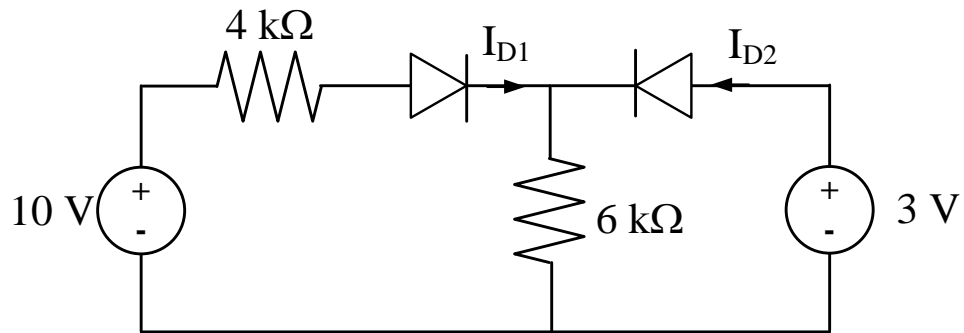


Problem Set 5 – Ideal Diodes Practice

- Find the current through each diode.

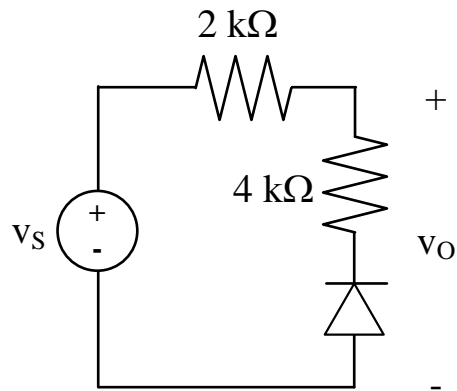

- Find the voltage, v_o given that $v_s = 8 \cos(\omega t)$ volts.



- Find the current through each diode and the voltage at points D and E relative to ground.

