
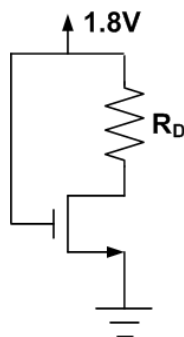


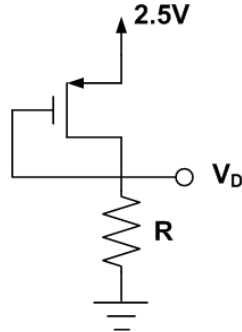
1. An NMOS transistor is characterized as follows: $V_{DS}=0.1V$, $V_t=1.5V$, $k'_n=25\ \mu A/V^2$, and $W/L=10$. Find the drain current for $V_{GS}=0V, 1V, 2V$, and $3V$.
2. An NMOS transistor is characterized as follows: $V_{DS}=3.3V$, $V_t=1V$, $k'_n=37.5\ \mu A/V^2$, and $W/L=10$. Find the drain current for $V_{GS}=0V, 1V, 2V$, and $3V$.
3. Identify the region of operation and the drain current for an NMOS transistor where the $k'_n=25\ \mu A/V^2$, $V_t=1V$ and $W/L=10$.
 - a. $V_{GS}=5V$ and $V_{DS}=6V$
 - b. $V_{GS}=0V$ and $V_{DS}=6V$
 - c. $V_{GS}=2V$ and $V_{DS}=2V$
 - d. $V_{GS}=2V$ and $V_{DS}=-0.5V$
4. An NMOS transistor has $V_t=0.8V$, $k'_n=0.05\ mA/V^2$, and $W/L=2$. The device is biased at $V_{GS}=2.5V$. Calculate the drain current and the resistance r_O for $V_{DS}=2V$ and $10V$ for
 - a. $\lambda=0$
 - b. $\lambda=0.02$
 - c. $V_A=35V$
5. An NMOS transistor has $V_t=0.8V$, $k'_n=0.05\ mA/V^2$, and $W/L=2$. The device is biased at $V_{GS}=2.5V$. If $V_{DS}=4V$ and $V_A=40V$,
 - a. Find λ .
 - b. Find the drain current for no channel length modulation.
 - c. Find the drain current assuming channel length modulation.
 - d. If the drain source voltage changes by $2V$, what is the corresponding change in the drain current.
6. A PMOS transistor has $k'_p=0.1\ mA/V^2$, $W/L=2$, $V_t=-2V$ and $V_{SG}=3V$. Find the region of operation and the drain current for:
 - a. $V_{SD}=0.5V$
 - b. $V_{SD}=2V$
 - c. $V_{SD}=5V$
7. Consider the following NMOS circuit where $V_t=0.5V$, $k'_n=0.4\ mA/V^2$, and $W/L=5$. If the circuit operates at the edge of saturation with a drain current of $1mA$, find the resistor, R_D .





8. Consider the following PMOS circuit where $V_t = -0.6\text{V}$, $k'_p = 250 \mu\text{A/V}^2$, and $L = 0.25 \mu\text{m}$. find the values required for W and R such that the drain current is 0.8mA and the drain voltage is 1.5V



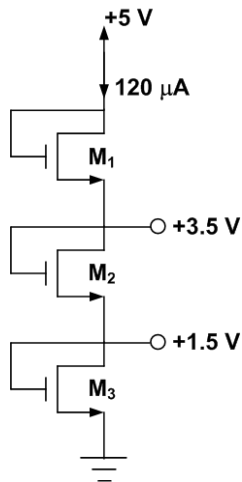
9. Consider the following circuit which contains three transistors that are matched with $V_t = 1\text{V}$, $k'_n = 120 \mu\text{A/V}^2$, and $L = 1 \mu\text{m}$. Find the gate width for each transistor for the given drain current and voltages.



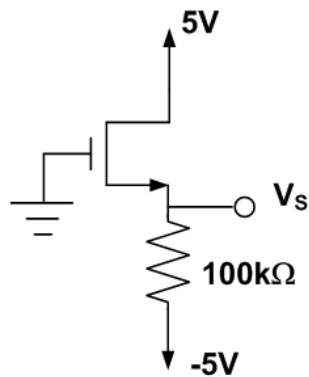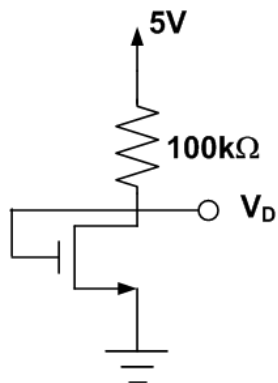10. Find the labeled voltages on the following circuits. For all the transistors, $V_t = 0.8\text{V}$, $k'_n = 0.25 \text{mA/V}^2$, and $W/L = 2$.



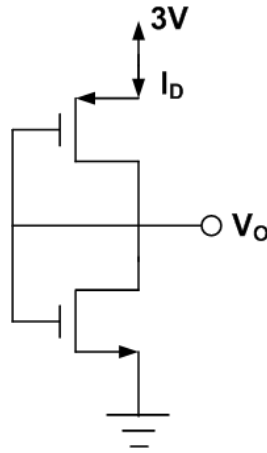11. Find the labeled voltages and currents in the following circuit where $V_{tn}=+1V$, $V_{tp}=-1V$, $k'_n=20\ \mu A/V^2$, $k'_p=8\ \mu A/V^2$ and $W/L=3$ (for both n and p-type transistors).



12. For the following circuit, find V_{DS} , V_{GS} , and I_D assuming $V_t=2V$, $k'_n=0.02\ mA/V^2$, and $W/L=5$.

