

Christopher Bero
CPE 322
Homework Simulation #2

Mealy Simulation

// Christopher Bero

// HW2 - Part 1 - Mealy FSM

module twos_complement(input Bin,clk,reset, output reg Bout);

reg [3:0] state,next_state;

parameter S0 = 0, S1 = 1, S2 = 2;

always @ (posedge clk)
begin

case (state)

S0:
begin
Bout = Bin;
if (Bin)
next_state = S2;
else
next_state = S1;
end

S1:
begin
Bout = 1;
if (Bin)
next_state = S1;
else
next_state = S2;
end

S2:
begin
Bout = ~Bin;
if (Bin)
next_state = S2;
else
next_state = S2;
end

endcase

if (reset)
begin
state = S0;
Bout = 0;
end

else
state = next_state;

```

end
endmodule

```

Stimulus

```

#
# Stimulus
# [0] is LSB
# SUB_ADD: 0=add (A+B), 1=subtract (A-B)
# Library: cycloneive_ver
#

#add list Bin reset clk Bout

#add wave Bin reset clk Bout

force Bin  0 0ns, 0 50ns, 1 100ns, 1 150ns, 0 200ns, 0 250ns, 1 300ns, 1 350ns, 0
400ns, 0 450ns, 1 500ns

force clk  0 0ns, 1 25ns, 0 50ns, 1 75ns, 0 100ns, 1 125ns, 0 150ns, 1 175ns, 0
200ns, 1 225ns, 0 250ns, 1 275ns, 0 300ns, 1 325ns, 0 350ns, 1 375ns, 0 400ns, 1
425ns, 0 450ns, 1 475ns, 0 500ns, 1 525ns, 0 550ns, 1 575ns, 0 600ns, 1 625ns, 0
650ns, 1 675ns, 0 700ns, 1 725ns, 0 750ns, 1 775ns, 0 800ns, 1 825ns, 0 850ns, 1
875ns


force reset 1 0ns, 0 50ns,
                                1 450ns, 0 500ns

run 1000ns

# Sample input:  01100110 1
# Returned output:      00111100 0

# Formatted:
# Original input:      1 01100110
# 2s complement:  1 10011011
# Program output:      0 00111100 <- incorrect output

```

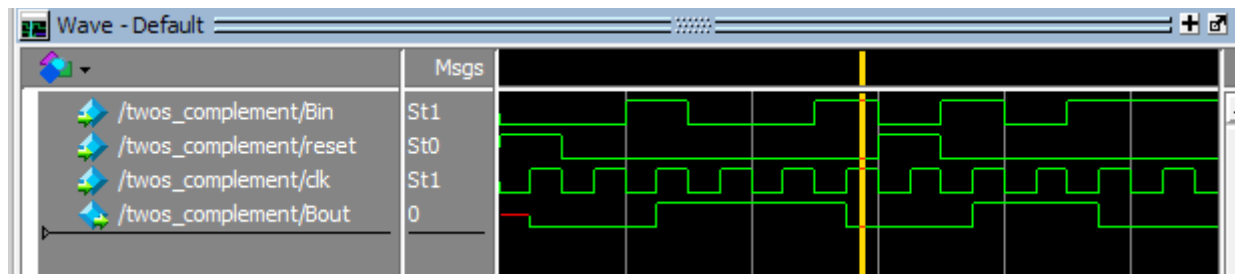

Moore Simulation

```

// Christopher Bero

```

```

// HW2 - Part 2 - Moore FSM
module moore_fsm(input Bin,clk,reset, output reg Bout);

    reg [3:0] state,next_state;

    parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3, S4 = 4;

    always @ ( posedge clk)
    begin
        case (state)

            S0:
            begin
                Bout = 0;
                if (Bin)
                    next_state = S3;
                else
                    next_state = S1;
            end

            S1:
            begin
                Bout = 0;
                if (Bin)
                    next_state = S2;
                else
                    next_state = S3;
            end

            S2:
            begin
                Bout = 1;
                if (Bin)
                    next_state = S2;
                else
                    next_state = S3;
            end

            S3:
            begin
                Bout = 1;
                if (Bin)
                    next_state = S4;
                else
                    next_state = S3;
            end

            S4:
            begin
                Bout = 0;
                if (Bin)
                    next_state = S4;
                else
                    next_state = S3;
            end

        endcase
    end

```

```

        if (reset)
            begin
                state = S0;
                Bout = 0;
            end
        else
            state = next_state;
        end
    end

endmodule

#
# Stimulus
# [0] is LSB
# SUB_ADD: 0=add (A+B), 1=subtract (A-B)
# Library: cycloneive_ver
#

#add list Bin reset clk Bout

#add wave Bin reset clk Bout

force Bin  0 0ns, 0 50ns, 1 100ns, 0 150ns, 0 200ns, 1 250ns, 0 300ns, 1 350ns, 0
400ns, 1 450ns

force clk  0 0ns, 1 25ns, 0 50ns, 1 75ns, 0 100ns, 1 125ns, 0 150ns, 1 175ns, 0
200ns, 1 225ns, 0 250ns, 1 275ns, 0 300ns, 1 325ns, 0 350ns, 1 375ns, 0 400ns, 1
425ns, 0 450ns, 1 475ns, 0 500ns, 1 525ns, 0 550ns, 1 575ns, 0 600ns, 1 625ns, 0
650ns, 1 675ns, 0 700ns, 1 725ns, 0 750ns, 1 775ns, 0 800ns, 1 825ns, 0 850ns, 1
875ns

force reset 1 0ns, 0 50ns,
           1 300ns, 0 350ns

run 1000ns

# Sample input:  01001 101
# Returned output:      01110 010

# Formatted:
# Original input:      101 10010
# 2s complement: 011 01111
# Program output:      011 01110 <- incorrect output

```

