

Lab 02 Report
Christopher Bero
EE 316

Inverting and Noninverting OP-Amp Circuits

Introduction

In this lab we continued to practice using MultiSim while creating and analyzing the impact of resistance values on standard OpAmp circuits.

Inverting OpAmp

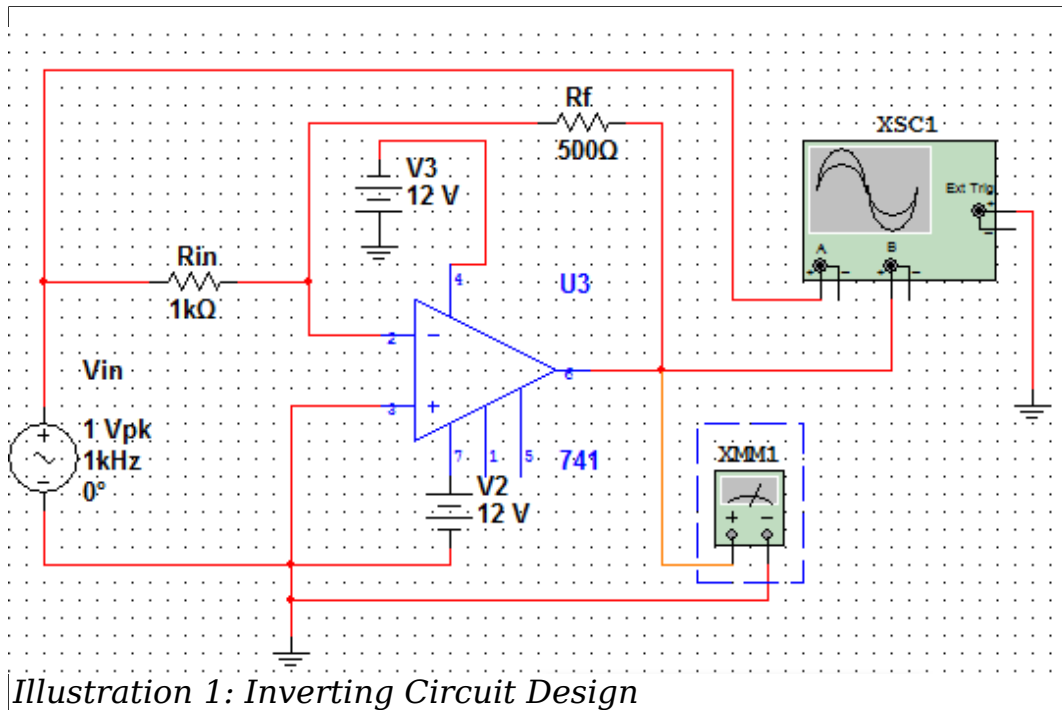


Illustration 1: Inverting Circuit Design

$V_{in} = 2V$; 1KHz; Inverting; $R_{in} = 1K$

R_f (k)	V_{out} (V)	Gain	V_{rms} (V)	Current (mA)
0.5	0.998	0.499	0.354	24.46
1	1.995	1.003	0.707	24.73
2	3.996	1.998	1.414	24.86
3	5.999	2.999	2.121	24.9
4	7.997	3.999	2.828	24.91

$V_{in} = 2V$; 100Hz; Inverting; $R_{in} = 1K$

R_f (k)	V_{out} (V)	Gain	V_{rms} (V)	Current (mA)
0.5	0.997	0.498	0.356	24.63
1	1.997	0.998	0.707	24.8
2	3.979	1.989	1.414	24.936
3	5.999	2.999	2.121	24.997
4	8	4	2.828	25.037

Noninverting OpAmp

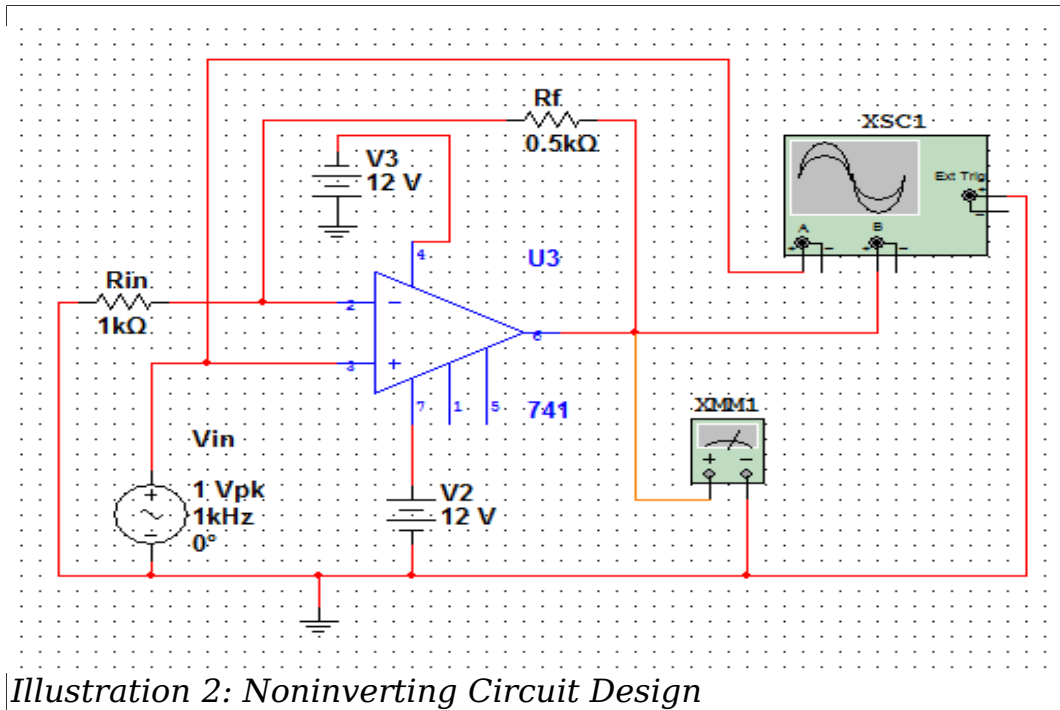


Illustration 2: Noninverting Circuit Design



$V_{in} = 2V$; 1KHz; Noninverting; $R_{in} = 1K$

R_f (k)	V_{out} (V)	Gain	V_{rms} (V)	Current (mA)
0.5	2.997	1.498	1.061	25.08
1	3.999	1.999	1.414	25.03
2	5.994	2.997	2.121	25.03
3	7.988	3.994	2.828	25.032
4	9.995	4.997	3.535	25.042



$V_{in} = 2V$; 100Hz; Noninverting; $R_{in} = 1K$

R_f (k)	V_{out} (V)	Gain	V_{rms} (V)	Current (mA)
0.5	2.994	1.497	1.061	25.177
1	3.996	1.998	1.414	25.179
2	5.999	2.999	2.121	25.18
3	8.036	4.018	2.828	25.173
4	9.994	4.997	3.535	25.18



Inverting OpAmp 1KHz - Oscilloscope

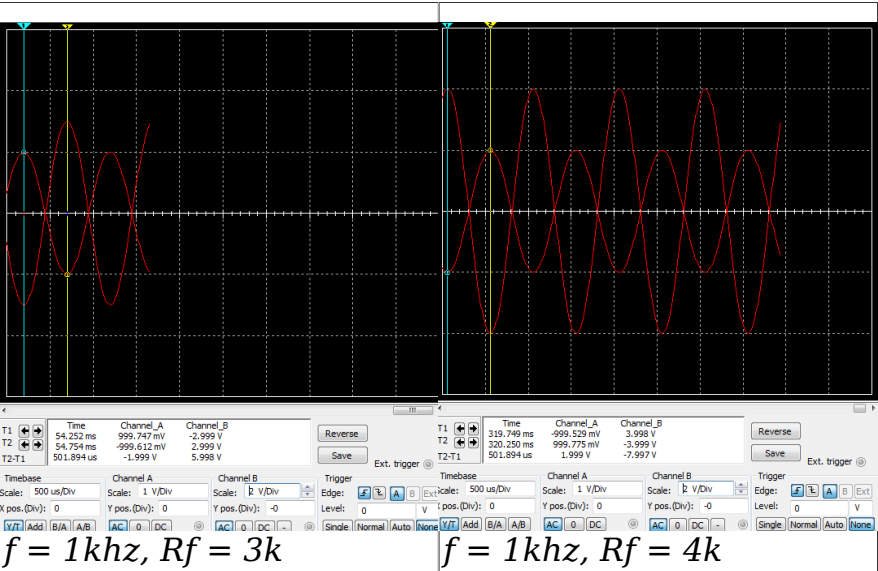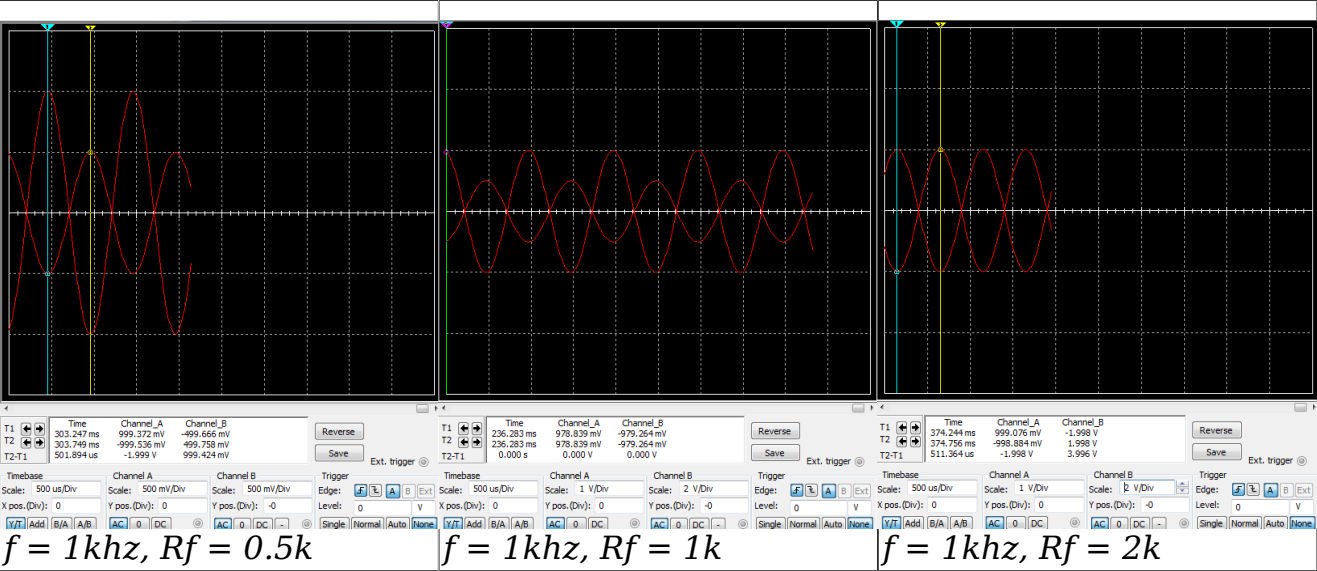



Inverting OpAmp 100Hz - Oscilloscope

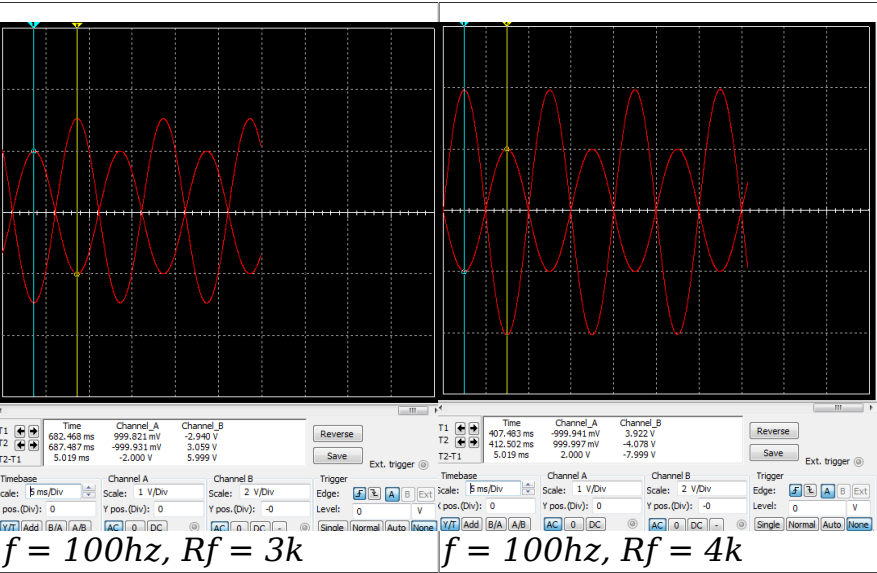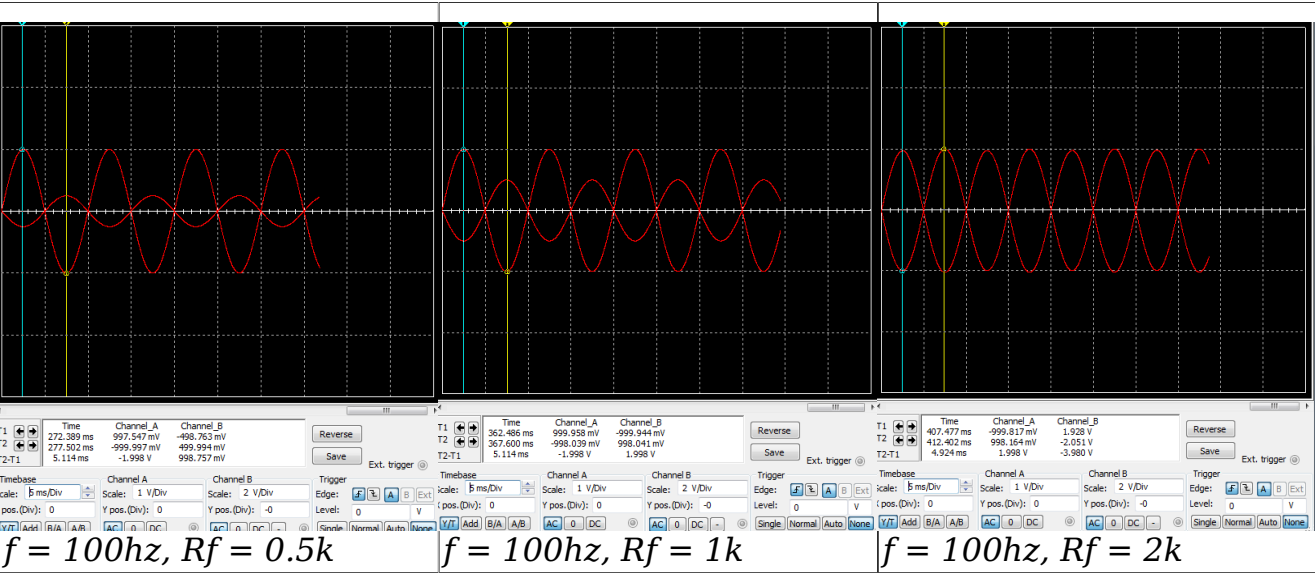

Noninverting OpAmp 1KHz - Oscilloscope

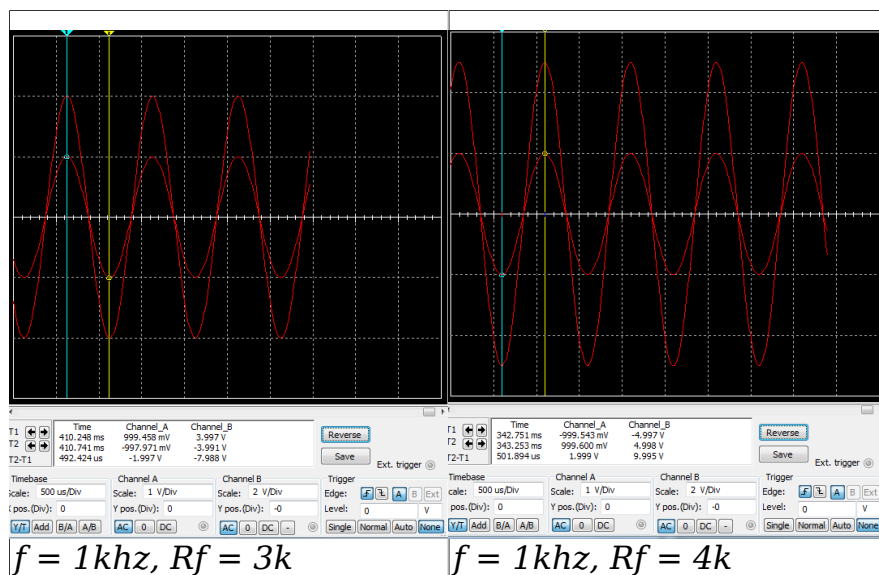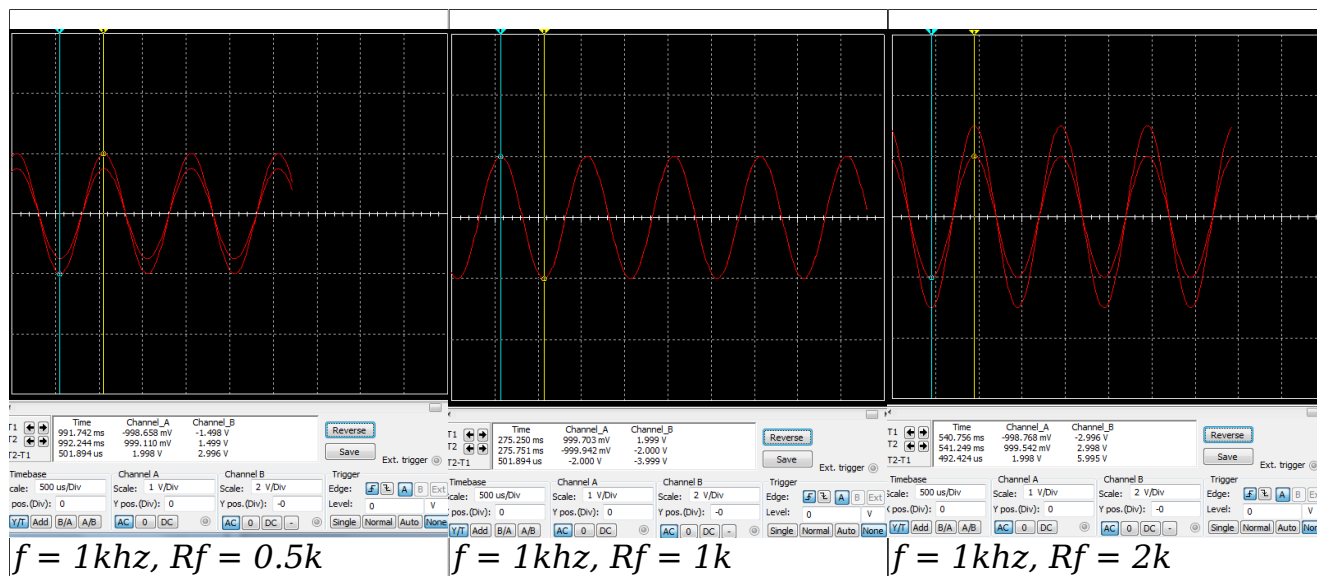

Inverting OpAmp 100Hz - Oscilloscope

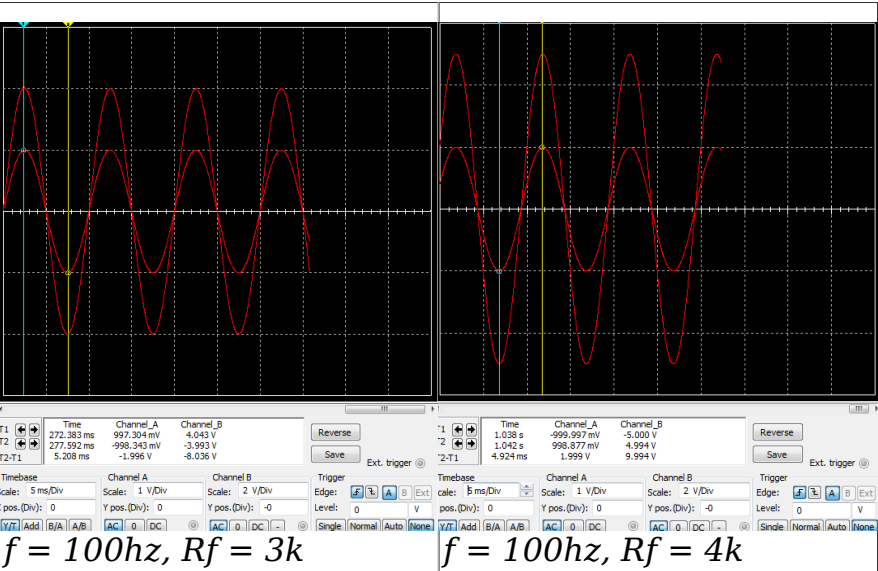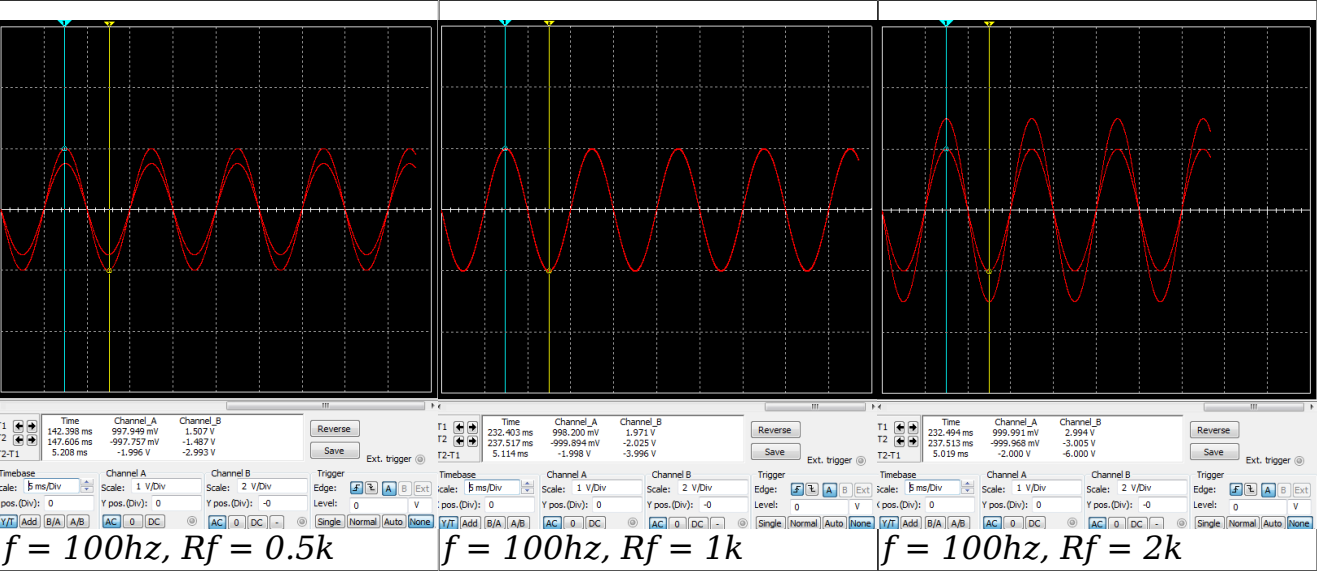

Simulation Results

Overall, the circuits behaved very much as expected based on our previous experience with the topic in class. We can see from the manipulation of R_f in both circuit designs that gain can be controlled very precisely to define this most important aspect of the system. Resistance had a very small impact on current, and input voltage frequency had negligible affect. Looking back at gain for both inverting and noninverting circuits, we can see that it is not changed by input voltage frequency. This leads us to conclude that the OpAmp 741 is capable of a wide range of input voltage frequencies as we have modulated ours by an order of magnitude.

Hardware

Our team (I paired with another student for this section) attempted to wire the first inverting configuration. We believe the design was correct, but were unable to get reasonable output from the OpAmp. The voltage supply is suspected of either incorrect configuration or insufficient supply.