CPE322 SIM 04 HW Christopher Bero

## texter control

```
module texter_control (clk, sw, dash_dit, dc_error, space, tm_reset,
nxt_char, back_sp, nxt_bit, sp_load, out_char, out_space);
input clk, sw, dash_dit, dc_error, space;
output tm_reset, nxt_char, back_sp, nxt_bit, sp_load, out_char,
out_space;
reg [2:0] state, nextstate;
reg tm_reset, nxt_char, nxt_bit, back_sp, sp_load, out_char,
out_space;
initial
begin
state = 0;
nextstate = 0;
tm_reset = 0;
nxt_char = 0;
nxt_bit = 0;
back_sp = 0;
sp_load = 0;
out_char = 0;
out\_space = 0;
end
always @(posedge clk)
begin
if (state == 0) begin
     if (sw) begin
          tm_reset = 1;
          nxt_char = 1;
          nextstate = 1;
          end
     else
          nextstate = 0;
end
else if (state == 1) begin
     if (sw) begin
          nextstate = 1;
     end
     else if (space) begin
     back\_sp = 1;
     nextstate = 1;
     end
     else begin
          nxt_bit = 1;
          if (dash_dit) begin
               sp_load = 1;
          end
          nextstate = 2;
     end
end
else if (state == 2) begin
```

```
tm\_reset = 1;
     nextstate = 3;
end
else if (state == 3) begin
     if (sw) begin
          sp_load = 1;
          nextstate = 4;
     end
     else begin
          if (dash_dit) begin
               if (dc_error) begin
                    nextstate = 0;
               end
               else begin
                    out_char = 1;
                    nextstate = 5;
               end
          end
          else begin
               nextstate = 3;
          end
     end
end
else if (state == 4) begin
     tm_reset = 1;
     nextstate = 1;
end
else if (state == 5) begin
     if (sw) begin
          nxt_char = 1;
          tm\_reset = 1;
          nextstate = 1;
     end
     else begin
          if (space) begin
               out_space = 1;
               nextstate = 0;
          end
          else begin
               nextstate = 5;
          end
     end
end
state = nextstate;
end
endmodule
```

## Stimulus

```
# Stimulus
# [0] is LSB
# SUB_ADD: 0=add (A+B), 1=subtract (A-B)
# Library: cycloneive_ver
#
#add list Bin reset clk Bout

#add wave Bin reset clk Bout

force dc_error 0 0, 1 800, 0 1000

force dash_dit 1 0, 0 50 -repeat 100

force space 0 0, 1 400 -repeat 800


force sw 1 0, 0 200 -repeat 400

force clk 0 0, 1 20 -repeat 40

run 4000
```

## Output

🐺 List - Default 💳					377	***						
ps	/texter_control/clk-	/texter_c	onti	col/tm_rese	et-y/te	ext	er_c	ontr	ol/out	char-		
delta-	/texter_control/	sw⊸, /text	er_c	control/nx	t_char	<b>-</b> /1	text	er_c	ontrol,	out_spac	e <b>-</b> -	
	/texter_control/da	sh_dit-	text	er_contro	l/back	_sp	₹	/	texter	_control/	state-	
	/texter_contro	l/dc_erro	r/	texter_co	ntrol/	nxt	bit	<b>→</b> /	texter	control/	nextstat	e⊸
	/texter	_control/	spac	e-v/texte	r_cont	rol,	/sp_	load	₹			
0 +0		St1 St1			0	0	0	0	0	0	0 000	
20 +0		St1 St1			1	1	0	0	0	0	0 001	
40 +0		St1 St1			1	1	0	0	0	0	0 001	
50 +0		St1 St0			1	1	0	0	0	0	0 001	
60 +0		St1 St0			1	1	0	0	0	0	0 001	
80 +0		St1 St0 St1 St1			1	1	0	0	0	0	0 001	
100 +0 120 +0		St1 St1			1	1	0	0	0	0	0 001	
140 +0		St1 St1			1	1	0	0	0	0	0 001	
150 +0		St1 St0			1	1	0	0	0	0	0 001	
160 +0		St1 St0			1	1	0	0	0	0	0 001	
180 +0		St1 St0			1	1	0	0	0	0	0 001	
200 +0	St0	St0 St1	St0	St0	1	1	0	0	0	0	0 001	001
220 +0	St1	St0 St1	St0	St0	1	1	0	1	1	0	0 010	010
240 +0	St0	St0 St1	St0	St0	1	1	0	1	1	0	0 010	010
250 +0	St0	St0 St0	St0	St0	1	1	0	1	1	0	0 010	010
260 +0	St1	St0 St0	St0	St0	1	1	0	1	1	0	0 011	011
280 +0	St0	St0 St0	St0	St0	1	1	0	1	1	0	0 011	011
300 +0		St0 St1			1	1	0	1	1	1	0 101	
320 +0		St0 St1			1	1	0	1	1	1	0 101 :	
340 +0		St0 St1			1	1	0	1	1	1	0 101	
350 +0		St0 St0 St0 St0			1	1	0	1	1	1	0 101	
360 +0 380 +0		StO StO			1	1	0	1	1	1	0 101 :	
400 +0		St1 St1			1	1	0	1	1	1	0 101	
420 +0		St1 St1			1	1	0	1	1	1	0 001	
440 +0		St1 St1			1	1	0	1	1	1	0 001	
450 +0	St0	St1 St0	St0	St1	1	1	0	1	1	1	0 001	001
460 +0	St1	St1 St0	St0	St1	1	1	0	1	1	1	0 001	001
480 +0	St0	St1 St0	St0	St1	1	1	0	1	1	1	0 001	001
500 +0		St1 St1			1	1	0	1	1	1	0 001	
520 +0		St1 St1			1	1	0	1	1	1	0 001	001
540 +0		St1 St1			1	1	0	1	1	1	0 001	
550 +0		St1 St0			1	1	0	1	1	1	0 001	
560 +0		St1 St0			1	1	0	1	1	1	0 001	
580 +0		St1 St0			1	1	0	1	1	1	0 001	
600 +0 620 +0		St0 St1 St0 St1			1	1	0	1	1	1	0 001	
640 +0		St0 St1			1	1	1	1	1	1	0 001	
650 +0		St0 St1			1	1	1	1	1	1	0 001	
660 +0		St0 St0			1	1	1	1	1	1	0 001	
680 +0		St0 St0			1	1	1	1	1	1	0 001	
700 +0		St0 St1			1	1	1	1	1	1	0 001	
720 +0		St0 St1			1	1	1	1	1	1	0 001	
740 +0	St1	St0 St1	St0	St1	1	1	1	1	1	1	0 001	001
750 +0	St1	St0 St0	St0	St1	1	1	1	1	1	1	0 001	001

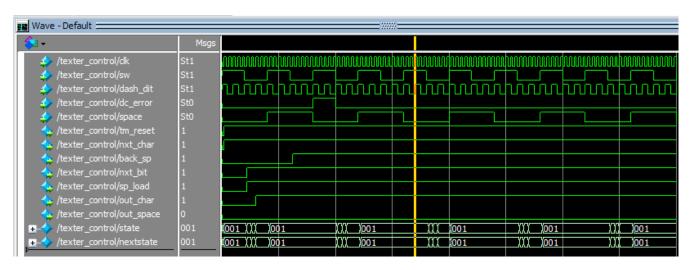

Flow Status Successful - Tue Apr 28 10:19:52 2015 Ouartus II 32-bit Version 13.0.1 Build 232 06/12/2013 SP 1 SJ Full Version Revision Name texter\_control Top-level Entity Name texter\_control Family Cyclone IV E Device EP4CE115F29C7 Timing Models Final Total logic elements 2 / 114,480 ( < 1 % ) Total combinational functions 2 / 114,480 ( < 1 %) Dedicated logic registers 2 / 114,480 ( < 1 % ) Total registers 2 Total pins 12 / 529 (2%) Total virtual pins 0 Total memory bits 0 / 3,981,312 (0 %) Embedded Multiplier 9-bit elements 0 / 532 (0 %) Total PLLs 0/4(0%)