


Lab 10 Report
Christopher Bero
EE 316

Amplification of a Signal Using JFETs


Simulation

The simulation portion of this assignment had us model a circuit from the following layout and test its output voltage against a variety of input frequencies. This shows us how the JFET will respond to a given bandwidth, or range of frequencies.

Circuit Model

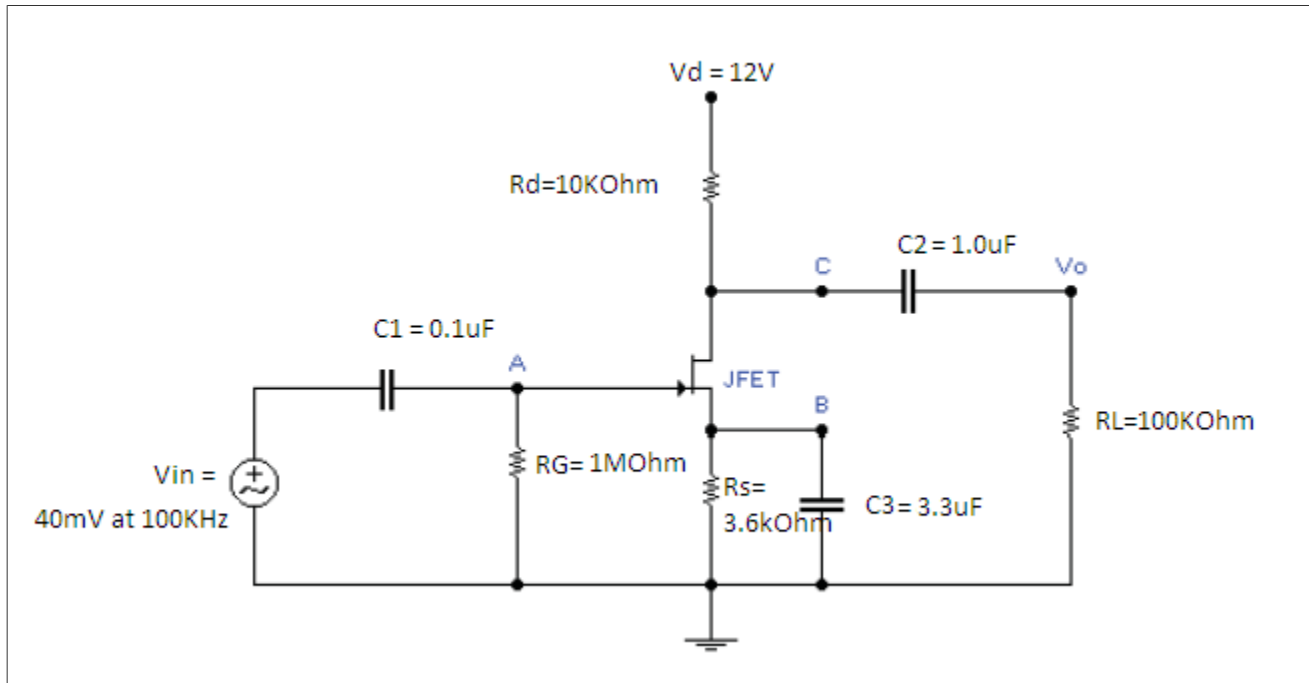


Simulation Circuit

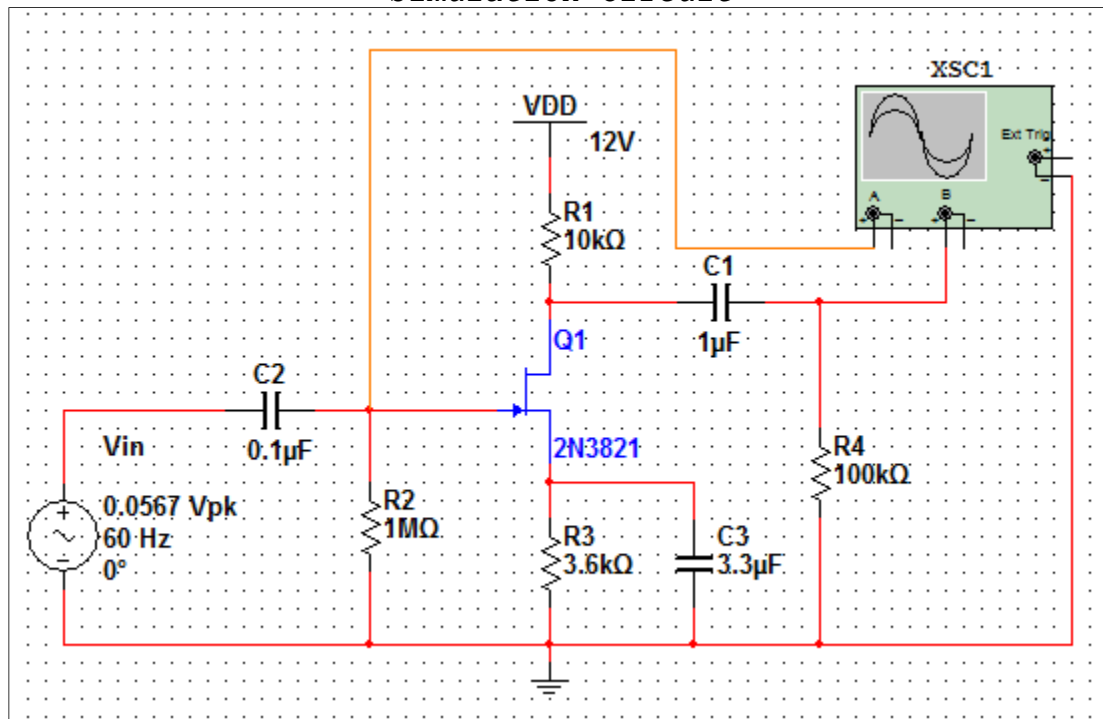


Circuit Responses


10Hz

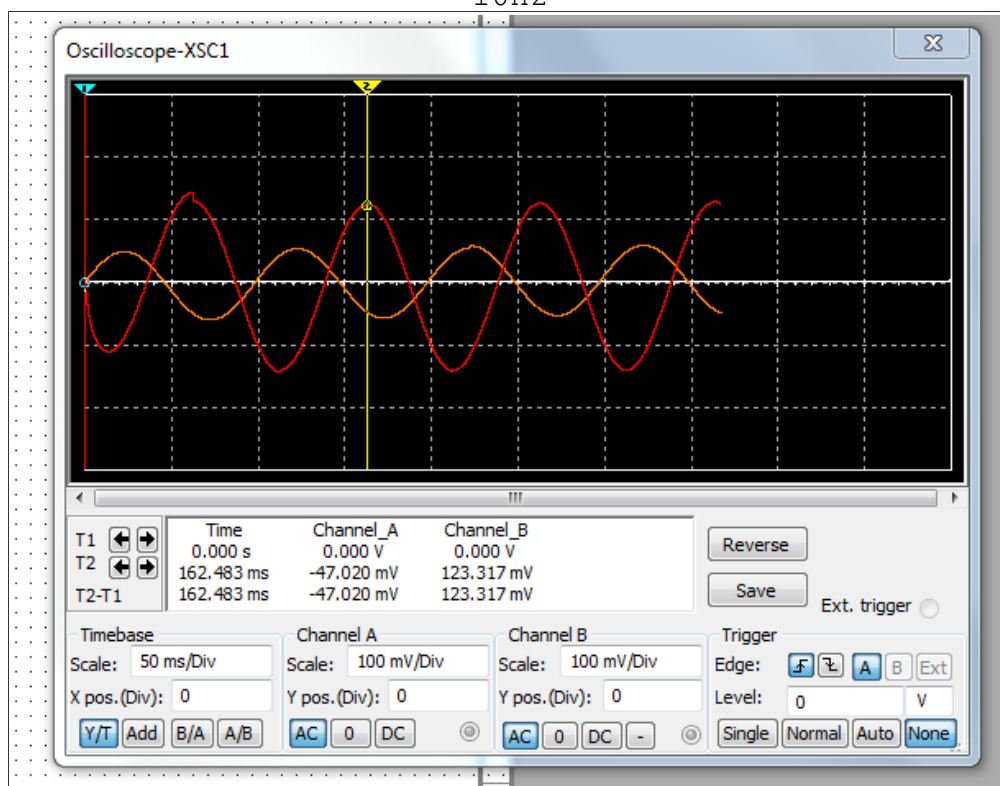


30Hz

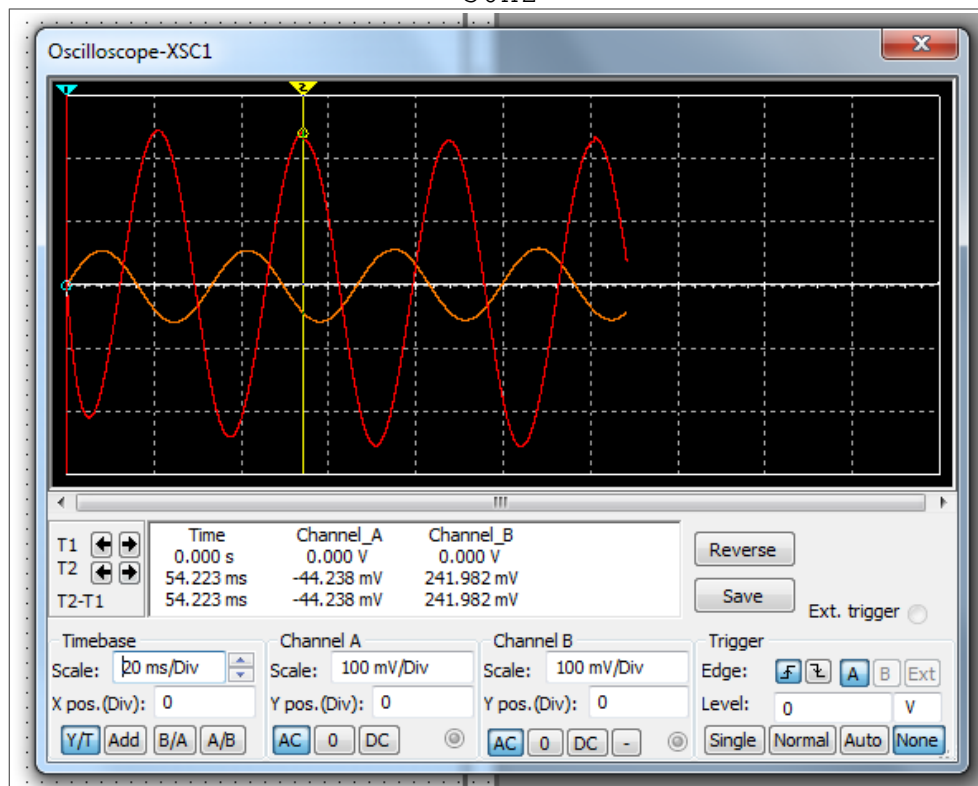


60Hz

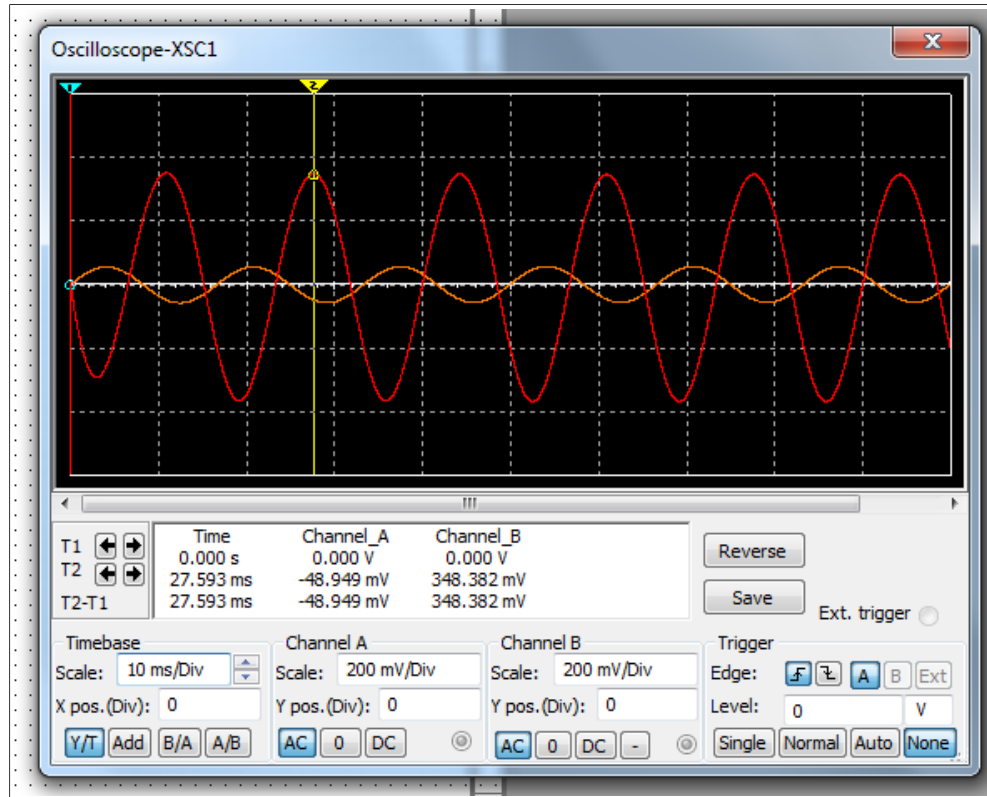

1.5KHz

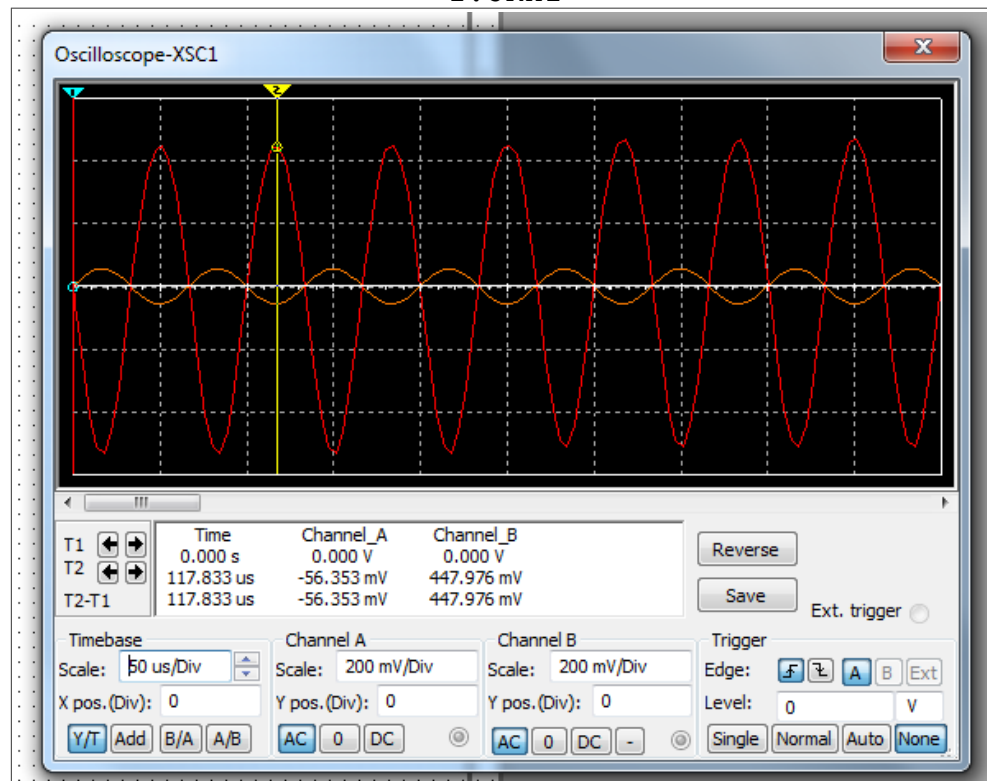


15KHz

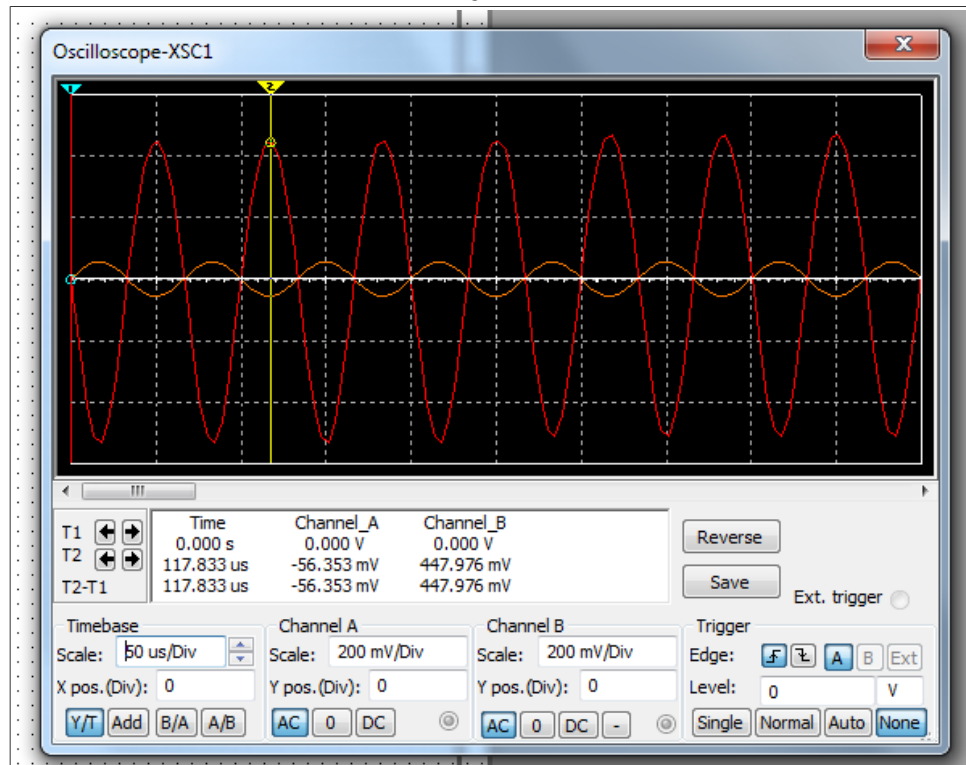

Simulation Results

Frequency	Vout (Vpk)	Voltage Gain
10	0.123317	2.18
30	0.241982	4.27
60	0.348382	6.14
100	0.409094	7.22
200	0.451050	7.96
500	0.467524	8.25
1 KHz	0.465341	8.21
2 kHz	0.459702	8.11
5 KHz	0.451954	7.97
10 KHz	0.448771	7.91
15 KHz	0.447976	7.9
20 KHz	0.447574	7.89
50 KHz	0.446900	7.88
75 KHz	0.446820	7.88
100 KHz	0.446822	7.88
150 KHz	0.446905	7.88
200 KHz	0.447018	7.88
500 KHz	0.447529	7.89
750 KHz	0.447528	7.89
1 MHz	0.447117	7.89
1.5 MHz	0.445025	7.85
2.0 MHz	0.441252	7.78


Simulation Results

 

Hardware Results

Frequency	Vout (Vpk-pk)	Voltage Gain
10	0.191	1.68
30	0.334	2.95
60	0.490	4.32
100	0.595	5.25
200	0.680	6
500	0.710	6.26
1 KHz	0.720	6.35
2 kHz	0.720	6.35
5 KHz	0.710	6.26
10 KHz	0.700	6.17
15 KHz	0.700	6.17
20 KHz	0.690	6.08
50 KHz	0.680	6
75 KHz	0.680	6
100 KHz	0.680	6
150 KHz	0.680	6
200 KHz	0.670	5.91
500 KHz	0.800	7.05
750 KHz	0.710	6.26
1 MHz	0.650	5.73
1.5 MHz	0.510	4.5
2.0 MHz	0.410	3.62

Hardware Results

 

Conclusion

The JFET circuit used has a very clean gain mapping, where a large area of the frequency spectrum is plateaued. The gain graphs between simulation and hardware circuits were surprisingly agreeable, each showing the same characteristics that we expect. Compared to the MOSFET used in an earlier lab, the JFET has a much larger bandwidth and more leveled gain rather than the ramp plot we see from Lab 08.