
# Voltage/current dividers

Trivial to understand, but still very useful.

Use in combination with equivalent resistances to quickly find a particular voltage or current in a circuit.

#### Voltage divider

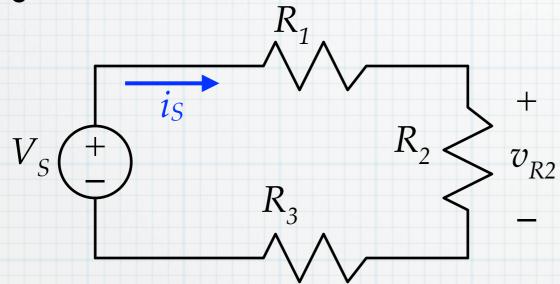

$$i_S = rac{V_S}{R_{eq}}$$


$$= rac{V_S}{R_1 + R_2 + R_3}$$

Want to know  $v_{R2}$ .

Easily solved with KCL, KVL, & equivalent resistances.

$$v_{R2}=i_SR_2$$
 
$$= \frac{R_2}{R_1+R_2+R_3}V_S \quad \text{That's it.}$$

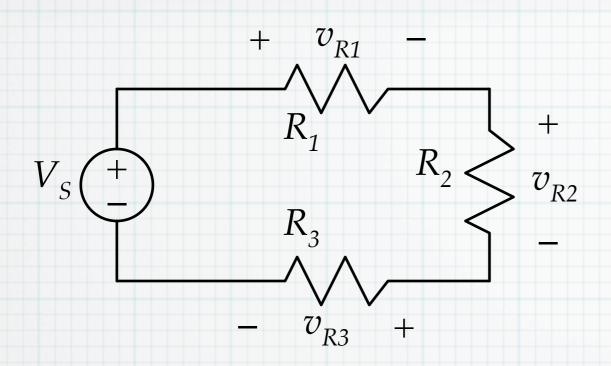The total voltage across a series string is divided among the resistors according to a simple ratio.




Easy to find the other voltages, too.

$$v_{R1} = \frac{R_1}{R_1 + R_2 + R_3} V_S$$

$$v_{R3} = \frac{R_3}{R_1 + R_2 + R_3} V_S$$

Put in some values.

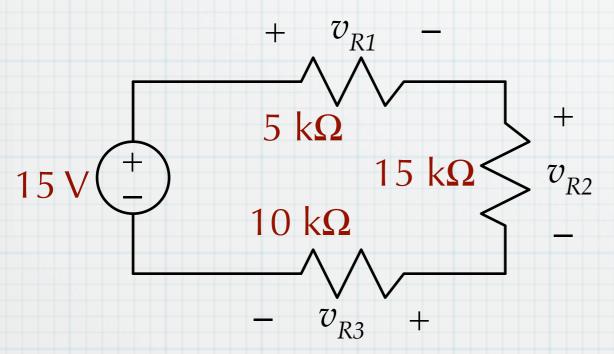


$$v_{R1} = \frac{5k\Omega}{5k\Omega + 15k\Omega + 10k\Omega} (15V) = 2.5V$$

$$v_{R2} = \frac{15k\Omega}{5k\Omega + 15k\Omega + 10k\Omega} (15V) = 7.5V$$

$$v_{R3} = \frac{10k\Omega}{5k\Omega + 15k\Omega + 10k\Omega} (15V) = 5V$$

#### Current divider

Same idea, but with current.

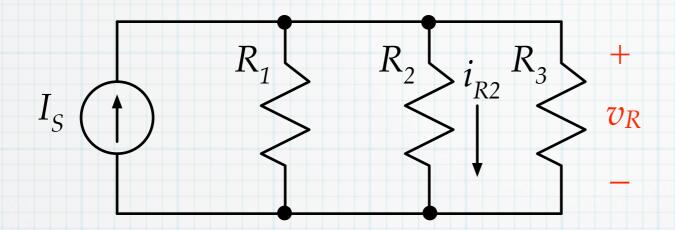


Want to know  $i_{R2}$ .

Easily solved with KCL, KVL, & equivalent resistances.

$$v_R = I_S R_{eq}$$
  $i_{R2} = \frac{v_R}{R_2}$   $= \frac{I_S}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} I_S$ 

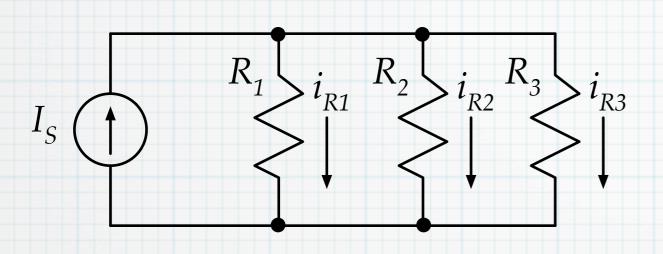
The total is divided according a simple ratio determined by the resistors.



The other currents are just as easy.

$$i_{R1} = \frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} I_S$$
 $i_{R3} = \frac{\frac{1}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_2}} I_S$ 

Plug in some numbers.

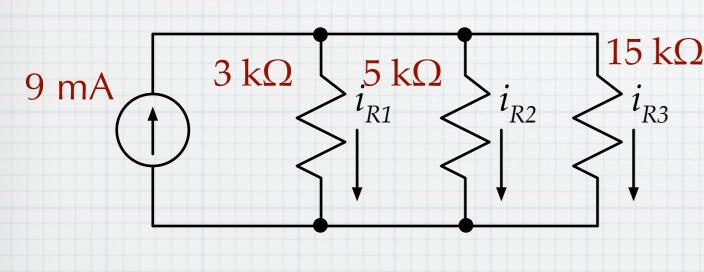


$$i_{R1} = \frac{\frac{1}{3k\Omega}}{\frac{1}{3k\Omega} + \frac{1}{5k\Omega} + \frac{1}{15k\Omega}} (9\text{mA}) = 5\text{mA}$$

$$i_{R1} = \frac{\frac{1}{3k\Omega}}{\frac{1}{3k\Omega} + \frac{1}{5k\Omega} + \frac{1}{15k\Omega}} (9mA) = 5mA$$

$$i_{R2} = \frac{\frac{1}{5k\Omega}}{\frac{1}{3k\Omega} + \frac{1}{5k\Omega} + \frac{1}{15k\Omega}} (9mA) = 3mA$$

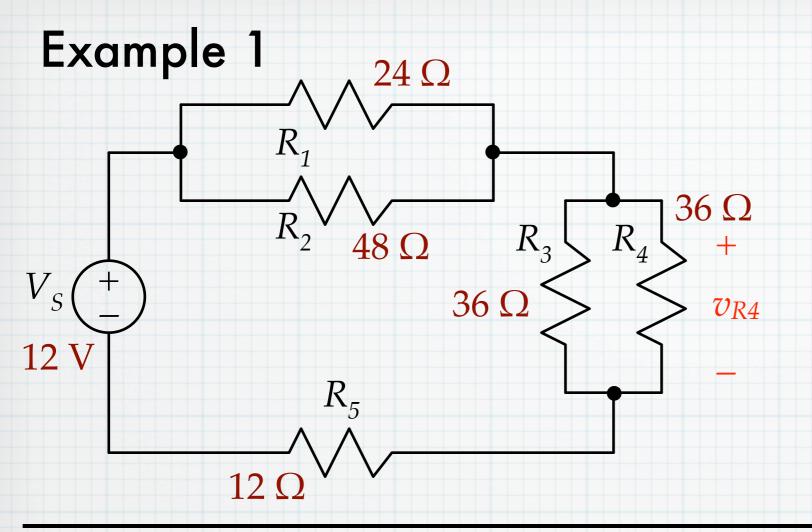
$$i_{R3} = \frac{\frac{1}{15k\Omega}}{\frac{1}{3k\Omega} + \frac{1}{5k\Omega} + \frac{1}{15k\Omega}} (9mA) = 1mA$$



In the circuit, find  $v_{R4}$ .

$$v_{R4} = v_{R3}$$

Combine parallel combinations.

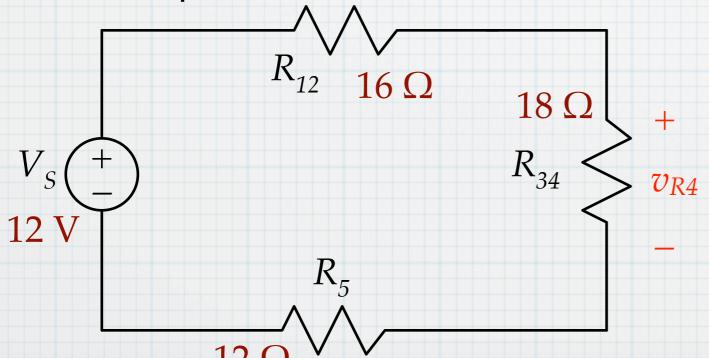


Use voltage divider.

$$v_{R4} = \frac{R_{34}}{R_{12} + R_{34} + R_5} V_S$$

$$= \frac{18\Omega}{16\Omega + 18\Omega + 12\Omega} (12V)$$

$$= 4.69V$$

## Example 2

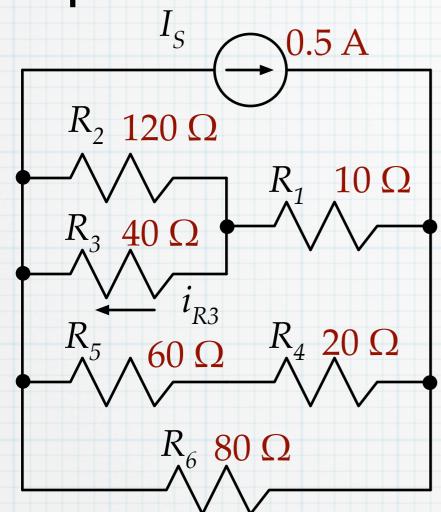


In the circuit, find  $i_{R3}$ .

Use a current divider to find  $i_{R13}$ .

$$i_{R13} = \frac{\frac{\frac{1}{R_{13}}}{\frac{1}{R_{13}} + \frac{1}{R_{45}} + \frac{1}{R_6}} I_S$$

$$= \frac{\frac{1}{40\Omega}}{\frac{1}{40\Omega} + \frac{1}{80\Omega} + \frac{1}{80\Omega}} (0.5A) = 0.25A$$

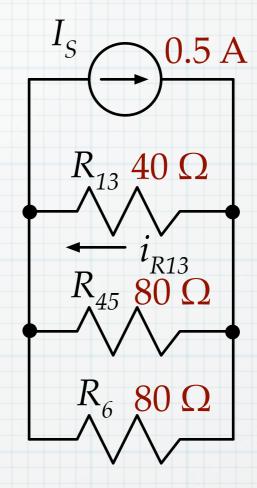Find the equivalent resistance in each branch.




Referring back to the original circuit,  $i_{R13}$  divides between  $R_2$  and  $R_3$ .

$$i_{R3} = rac{rac{1}{R_3}}{rac{1}{R_2} + rac{1}{R_3}} i_{R13}$$

$$= rac{rac{1}{40\Omega}}{rac{1}{120\Omega} + rac{1}{40\Omega}} (0.25A) = 0.1875A$$
voltage/current dividers – 6

EE 201

## Example 3

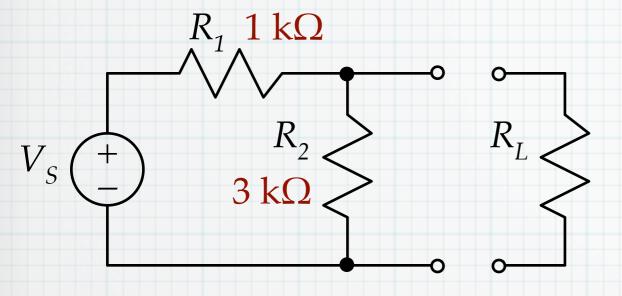

In the simple divider circuit at right, if  $R_L$  is attached in parallel with  $R_2$ , the voltage across  $R_1$  doubles. What is the value of  $R_L$ ?

Without  $R_L$ ,

$$v_{R1} = \frac{R_1}{R_1 + R_2} V_S$$

With  $R_L$ ,

$$v'_{R1} = rac{R_1}{R_1 + R_{eq}} V_S$$

$$= 2 rac{R_1}{R_1 + R_2} V_S$$

From the two expressions for  $v'_{R1}$ 


$$rac{R_1}{2} + rac{R_2}{2} = R_1 + R_{eq}$$
 $R_{eq} = rac{R_2 - R_1}{2} = rac{3k\Omega - 1k\Omega}{2} = 1k\Omega$ 

Then

$$\frac{1}{R_{eq}} = \frac{1}{R_2} + \frac{1}{R_L}$$

$$R_L = \frac{1}{\frac{1}{R_{eq}} - \frac{1}{R_2}} = 1.5k\Omega$$

#### Example 4

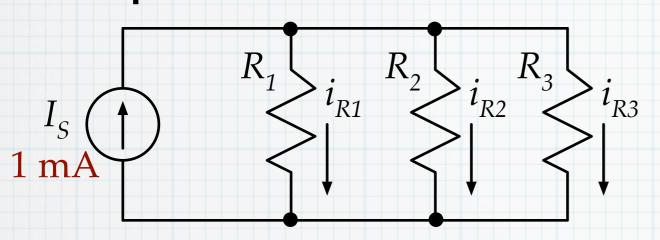

For the simple current divider at right, design it (i.e. choose resistor values) so that the currents are in the ratio  $i_{R1}:i_{R2}:i_{R3}=1:2:4$  and the total power dissipated in the resistors is 10 mW.

From the current divider equation, we know that the currents are proportional to the inverse of the resistance in each branch.

$$\frac{1}{R_1}: \frac{1}{R_2}: \frac{1}{R_3} = 1:2:4$$

Therefore,

$$R_1: R_2: R_3 = 4:2:1$$

$$R_2 = 2R_3$$
 and  $R_1 = 2R_2$  ( $R_1 = 4R_3$ ).

The equivalent resistance of the three in parallel is

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$= \frac{1}{4R_3} + \frac{1}{2R_3} + \frac{1}{R_3} = \frac{1.75}{R_3}$$

$$R_{eq} = \frac{R_3}{1.75}$$

Find 
$$R_{eq}$$
,
$$P = I_S^2 R_{eq} \longrightarrow R_{eq} = \frac{P}{I_S^2} = 10 \text{k}\Omega$$

Finally:

$$R_3 = 1.75R_{eq} = 17.5 \text{ k}\Omega$$
;  $R_2 = 2R_3 = 35 \text{ k}\Omega$ ;  $R_1 = 2R_2 = 70 \text{ k}\Omega$