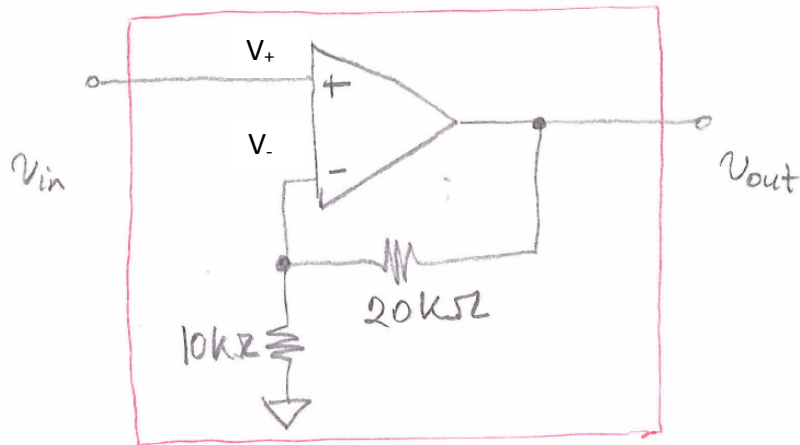


CPE 381: Fundamentals of Signals and Systems  
for Computer Engineers


## Homework #2 Solution

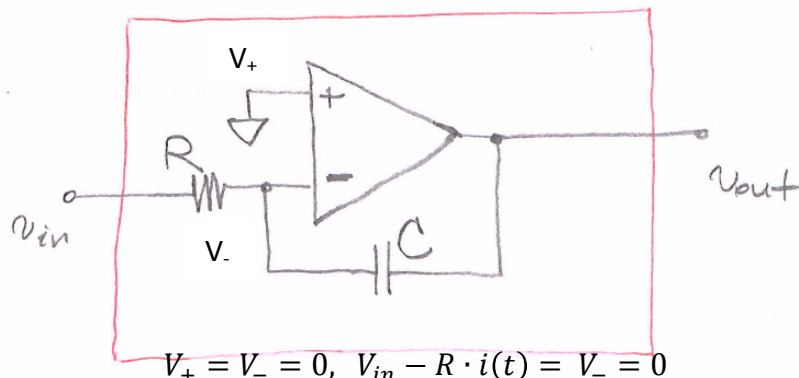1. (10 points) What is the transfer function of the following circuits



$$V_{in} = V_+ = V_- = \frac{R_1}{R_1 + R_2} V_{out}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_1 + R_2}{R_1} = 1 + \frac{R_2}{R_1} = 3$$



$$V_+ = V_- = 0, \quad V_{in} - R \cdot i(t) = V_- = 0$$

$$i(t) = \frac{V_{in}(t)}{R}$$

$$V_{out} = V_- - \frac{1}{C} \int_0^t i(\tau) d\tau + V_C^0 = -\frac{1}{C} \int_0^t \frac{V_{in}(\tau)}{R} d\tau = -\frac{1}{RC} \int_0^t V_{in}(\tau) d\tau$$

For unit-step function  $V_{in}$  is constant and


$$\frac{V_{out}}{V_{in}} = -\frac{t}{RC}$$

2. (20 points) Shift in time is equivalent to the shift in array. Therefore, shift of  $\tau$  seconds is equivalent to shift of  $M$  samples.


For sampling frequency  $F_s$ , sample interval is  $dt = 1/F_s$  and

$$M = \tau / dt = \tau F_s$$

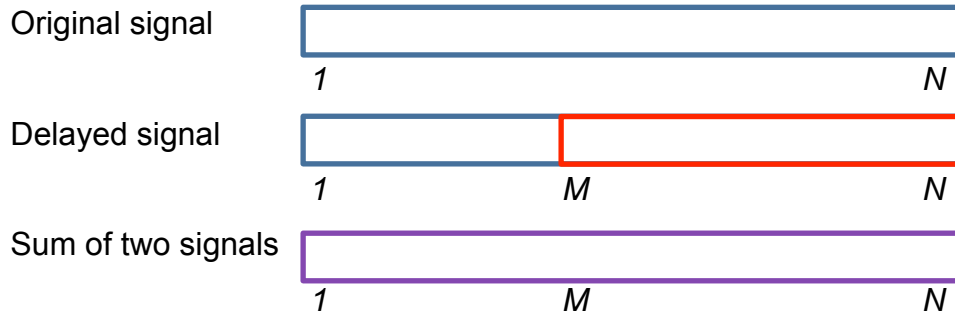In our case  $F_s = 8,192$  Hz,  $\tau = 0.5$  s is equivalent to  $M = 0.5 * 8,192 = 4,096$  samples.



```
% CPE381 HW2_1
load handel
N=length(y);           % length of sound array
% time
dt=1./Fs;
t=(1:N)*dt;
tau=0.5;               % delay in seconds [s]
Ndelay=round(Fs*tau);  % shift in samples
y1=[zeros(Ndelay,1); y(1:(N-Ndelay))]; % signal delayed for tau
y2=[zeros(2*Ndelay,1); y(1:(N-2*Ndelay))]; % signal delayed for 2*tau
% final output
yy=y+0.8*y1+0.5*y2;
figure
subplot(211)
plot(t,y)
subplot(212)
plot(t,yy),axis([0 9 -1 1])
title('x(t) + 0.8*x(t-tau) + 0.5*x(t-2*tau)')
% you can even hear the result!
sound(yy)
```

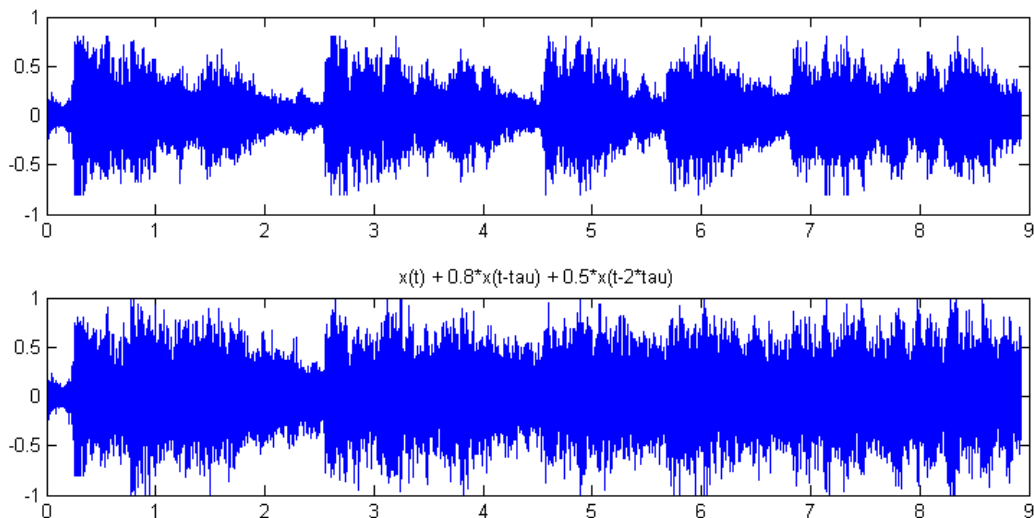

3. (10 points)

**Example** Find (i) impulse response of capacitor and (ii) its unit step response.  
 $C = 1 \text{ F}$ .

C:  $v_c(0) = 0$ ,

$$v_c(t) = \frac{1}{C} \int_0^t i(\tau) d\tau$$

Impulse response:

$$i(t) = \delta(t) \Rightarrow v_c(t) = h(t) = \frac{1}{C} \int_0^t \delta(\tau) d\tau = \frac{1}{C} u(t)$$

$C = 1\text{F}$ , unit-step response

$$v_c(t) = \int_{-\infty}^{\infty} h(t - \tau) i(\tau) d\tau = \int_{-\infty}^{\infty} \frac{1}{C} u(t - \tau) u(\tau) d\tau$$

$$v_c(t) = \frac{1}{C} \int_0^t d\tau = \frac{1}{C} r(t)$$

---

4. (15 points) Find transfer function of the circuit in problem 1.b.

If we use complex impedance  $Z_c$ , output will be

$$V_{out} = V_- - Z_c I = -\frac{1}{Cs} \cdot \frac{V_{in}}{R}$$

$$\frac{V_{out}}{V_{in}} = H(s) = -\frac{1}{RCs}$$


## 5. (20 points)

```
%CPE381: HW2_3

syms t x1 x2
x1=5*exp(-2*t)*cos(8*t)*heaviside(t);
x2=5*exp(-4*t)*cos(8*t)*heaviside(t);

X1=laplace(x1)
% X1 = 5*(s+2)/(s^2+4*s+68)
% plot
splane([5 10],[1 4 68])

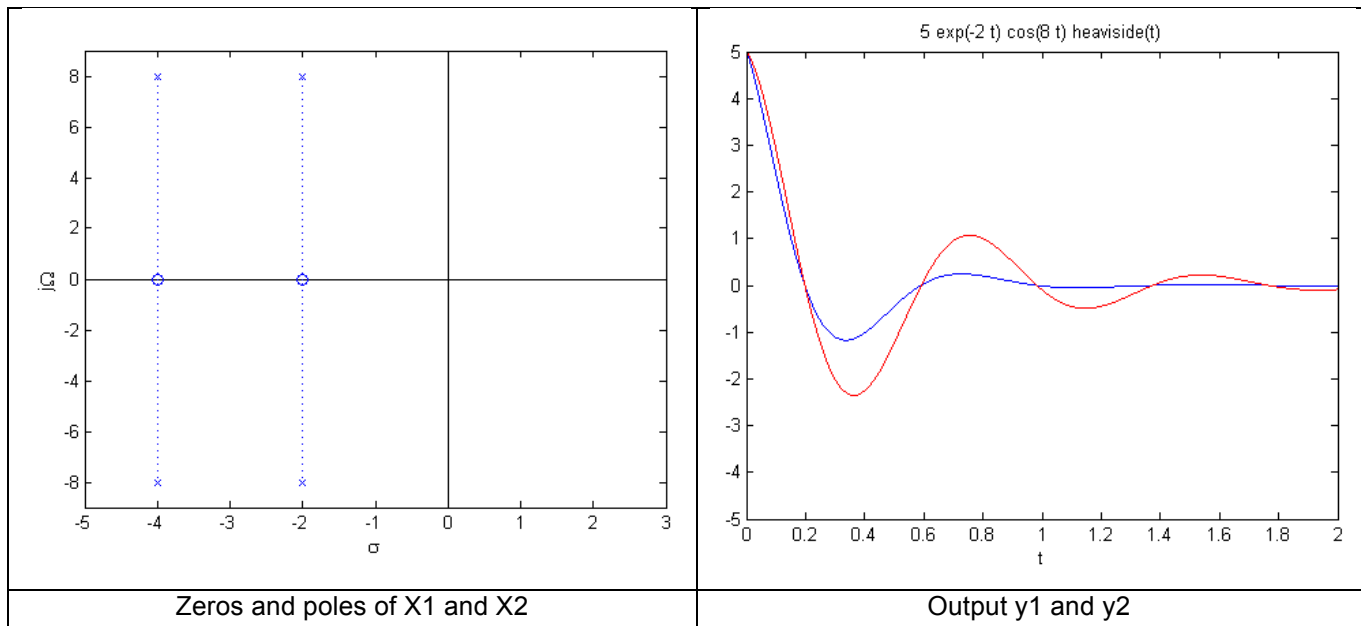X2=laplace(x2)
% X2 = 5*(s+4)/(s^2+8*s+80)
figure
% plot
splane([5 20],[1 8 80])
```




Discuss the changes in the s plane and describe their effect on function in time domain

Zeros and poles shifted to the left (larger absolute values of  $\sigma$ ); consequently, signal in time domain is more attenuated (damped).

6. (10 points)

Causal functions and constants:	$\alpha f(t)$	$\Leftrightarrow$	$\alpha F(s)$
Linearity:	$\alpha f(t) + \beta g(t)$	$\Leftrightarrow$	$\alpha F(s) + \beta G(s)$
Time shifting:	$f(t - \alpha)$	$\Leftrightarrow$	$e^{-\alpha s} F(s)$
Frequency shifting:	$e^{\alpha t} f(t)$	$\Leftrightarrow$	$F(s - \alpha)$
Multiplication by t:	$tf(t)$	$\Leftrightarrow$	$-\frac{dF(s)}{ds}$
Derivative:	$\frac{df(t)}{dt}$	$\Leftrightarrow$	$sF(s) - f(0^-)$
Second derivative:	$\frac{d^2 f(t)}{dt^2}$	$\Leftrightarrow$	$s^2 F(s) - sf(0^-) - f^{(1)}(0)$
Integral:	$\int_{0^-}^t f(t') dt$	$\Leftrightarrow$	$\frac{F(s)}{s}$
Expansion/Contraction:	$f(\alpha t) \alpha \neq 0$	$\Leftrightarrow$	$\frac{1}{ \alpha } F\left(\frac{s}{\alpha}\right)$

7. (15 points) Example 3.13

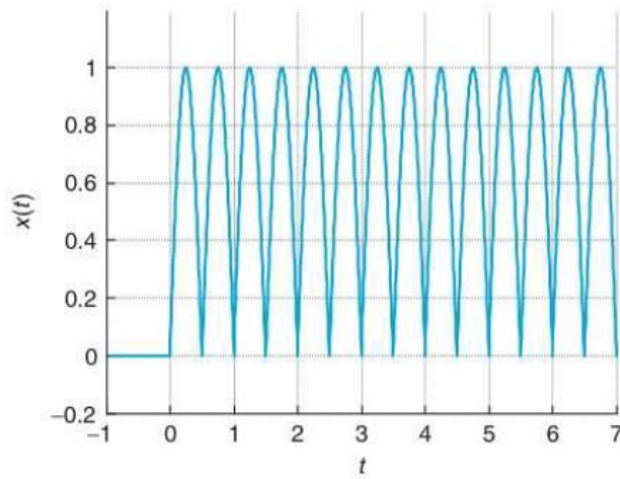

**FIGURE 3.13**

Full-wave rectified causal signal.

**Solution**

The first period of the full-wave rectified signal can be expressed as

$$x_1(t) = \sin(2\pi t)u(t) + \sin(2\pi(t - 0.5))u(t - 0.5)$$

and its Laplace transform is

$$X_1(s) = \frac{2\pi(1 + e^{-0.5s})}{s^2 + (2\pi)^2}$$

And the train of these sinusoidal pulses

$$x(t) = \sum_{k=0}^{\infty} x_1(t - 0.5k)$$

will then have the following Laplace transform:

$$X(s) = X_1(s)[1 + e^{-s/2} + e^{-s} + \dots] = X_1(s) \frac{1}{1 - e^{-s/2}} = \frac{2\pi(1 + e^{-s/2})}{(1 - e^{-s/2})(s^2 + 4\pi^2)}$$

